

BASIC ELECTRONICS
2nd Exam/ECE/CSE/IT/MECHATRONIC/0190/May'19
(FOR 2018 BATCH)

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Do as directed.

15x1=15

- a. Under normal operating voltages the reverse current in a silicon junction diode is in _____
- b. Ripple factor in full wave rectifier is _____
- c. CMOS means _____
- d. Write the relation between α and β .
- e. Biasing in transistor is done to stabilize the _____
- f. At absolute zero temperature an intrinsic semiconductor behaves like _____
- g. In saturation region both junctions of transistors are _____ Biased.
- h. When a P-N junction is heavily doped its breakdown voltage will _____
- i. Operation of JFET involves _____ carriers.
- j. Boron has _____ valence electrons.
- k. An ideal diode has _____ forward resistance.
- l. The ideal value of stability factor is _____
- m. The communication path in an FET through which the carriers flow between drain and source is called _____
- n. A capacitor circuit does not allow passing _____ component.
- o. The material used for the construction of LED is _____ band gap.\

SECTION-B

Q2. Attempt any five questions.

5x6=30

- i. Compare the MOSFET and BJT.
- ii. Explain the behavior of P-N junction under different bias conditions.
- iii. Draw h- model of CE amplifier.
- iv. Describe the importance of load line with suitable diagrams.
- v. Explain the terms avalanche and zener breakdown.
- vi. Give advantages and applications of CMOS.
- vii. Derive the relation $I_c = \alpha I_E + I_{CBO}$ and explain different terms used in them.
- viii. Write a note on drift and diffusion currents.
- ix. What is a filter circuit? Explain the working of LC filter.

SECTION-C

Q3. Attempt any three questions.

3x10=30

- a. Compare CB, CE and CC Configurations with at least five parameters.
- b. With the help of diagram and waveforms, Explain working of Center tap full wave rectifier.
- c. Explain the divider method of biasing for transistor (CE).
- d. Write a short note on any two of the following:
 - i. Thermal Runaway
 - ii. Varactor diode (Symbol, operation, application)
 - iii. BJT as an amplifier.
- e. Explain Construction, operation and characteristics of a MOSFET in depletion and enhancement modes.